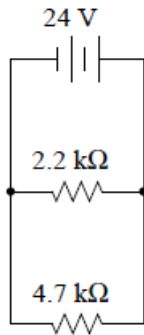


Name: \_\_\_\_\_ Block: \_\_\_\_\_


**Parallel DC Circuits**

1. Fill in the table for the following circuit. (Note that you can use  $V = IR$  directly with current in mA, resistance in  $k\Omega$  and power in mW.)




	R1	R2	Total
Voltage (V)	=	=	24
Current (mA)	+	=	
Resistance ( $k\Omega$ )	$\frac{1}{2.2}$	$\frac{1}{4.7}$	$\frac{1}{\quad}$
Power (mW)	+	=	

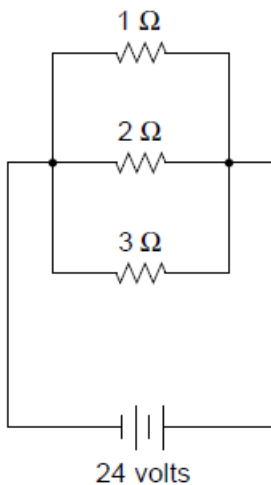2. Fill in the table for the following circuit:



	R1	R2	R3	Total
Voltage (V)				24
Current (A)				
Resistance ( $\Omega$ )	1	2	3	
Power (W)				

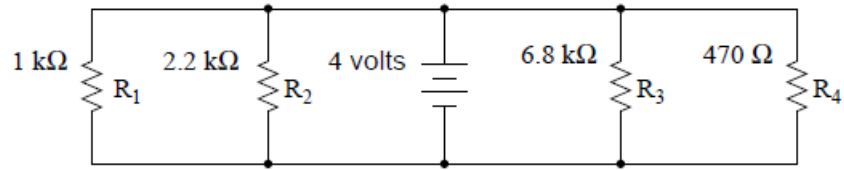3. Fill in the table for the following circuit.



	R1	R2	R3	R4	Total
Voltage (V)					4
Current (mA)					
Resistance (k $\Omega$ )	1	2.2	6.8	0.47	
Power (mW)					